

Homework 4

Danny Zou

12-03-2023

12.14.5

In the exercise, we examine in detail how an instruction is executed in singlecycle datapath. Problems in this exercise refer to a clock cycle in which the processor fetches the following instruction word: 0xadac0014.

(a) What are the values of the ALU control unit's inputs for this instruction?


ALU control units inputs are:

Opcode sw = 0010

ALUOp = 00

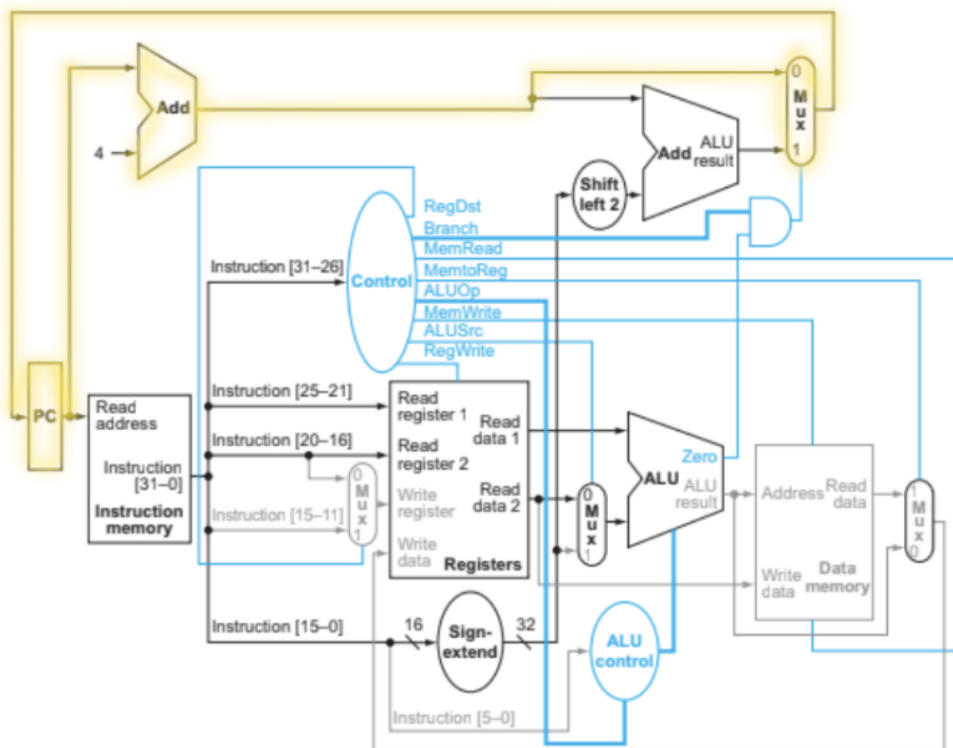(b) What is the new PC address after this instruction is executed? Highlight the path through which this value is determined.

The new PC address will be the current PC address + 4 because each instruction is 4 bytes and PC always points to the next instruction.



Path Highlighted in yellow

(c) For each mux, show the values of its inputs and outputs during the execution of this instruction. List values that are register outputs at Reg [xn]

There will be 3 muxes used.

ALUSrc

Inputs : Reg[t4] and 0x0014

Outputs : 0x0014

MemToReg

Inputs : Reg[t5] + 0x0014 and Undefined Input

Outputs : Undefined

Branch

Inputs : PC + 4 and PC + 0x28

Outputs : PC + 4

(d) What are the input values for the ALU and the two add units?

ALU

\$t5

0x0014

Two Add Units

PC + 4 Adder

-PC

-4

Branch Adder

-PC

-0x0028

(e) What are the values of all inputs for the registers unit?

Read Register 1 = 0x13

Read Register 2 = 0x12

Write Register = Doesn't Matter

Write Data = Doesn't Matter

RegWrite = False

12.14.7

(a) What is the latency of an R-type instruction(i.e., how long must the clock period be to ensure that this instruction works correctly)?

Latency of a R-Type Instruction = I-Mem/D-Mem + Register File + (2 * Mux) + ALU + Register Read + Register Setup

$$250ps + 150ps + (2 * 25ps) + 200ps + 30ps + 20ps = \boxed{700ps}$$

(b) What is the latency of lw? (Check your answer carefully. Many students place extra muxes on the critical path.)

Latency of Lw = Register Read + (2 * $I - Mem/D - Mem$) + Register File + ALU + (2 * Mux) + Register Setup

$$30ps + (2 * 250ps) + 150ps + 200ps + (2 * 25ps) + 20ps = \boxed{950ps}$$

(c) What is the latency of sw? (Check your answer carefully. Many students place extra muxes on the critical path.)

Latency of Sw = Register Read + (2 * $I - Mem/D - Mem$) + Register File + ALU + Mux

$$30ps + (2 * 250ps) + 150ps + 200ps + 25ps = \boxed{905ps}$$

(d) What is the latency of beq?

Latency of beq = Register Read + I-Mem/D-Mem + Register File + (2 * Mux) + ALU + Single Gate + Register Setup

$$30ps + 250ps + 150ps + (2 * 25ps) + 200ps + 5ps + 20ps = \boxed{705ps}$$

(e) What is the latency of an arithmetic, logical, or shift I-type (non-load) instruction?

Latency of I-type Instruction = Register Read + I-Mem/D-Mem + Register File + (2 * Mux) + ALU + Register Setup

$$30ps + 250ps + 150ps + (2 * 25ps) + 200ps + 20ps = \boxed{700ps}$$

(f) What is the minimum clock period for this CPU?

$$\text{Minimum Clock Speed} = \boxed{950ps}$$

12.14.10

(a) What is the speedup achieved by adding this improvement?

Clock Cycle Time before improvements = $250 + 150 + 25 + 200 + 150 + 5 + 30 + 20 + 50 + 50 = 930\text{ps}$

Clock Cycle Time after improvements = $250 + 160 + 25 + 200 + 150 + 5 + 30 + 20 + 50 + 50 = 940\text{ps}$

$25 - (25 * 0.12) = 22$

$52 + 22 + 11 + 12 = 97$ instructions after improvement

Speed up = $\frac{\frac{930}{100}}{\frac{930}{97}} \approx 0.96$

(b) Compare the change in performance to the change in cost.

Cost before improvements = $1000 + 200 + 10 + 100 + 30 + 2000 + 5 + 100 + 1 + 500 = 3946$

Cost per unit clock cycle before improvement = Cost / Clock cycle time = $\frac{3946}{930} = 4.24$

Cost after improvements = $1000 + 400 + 10 + 100 + 30 + 2000 + 5 + 100 + 1 + 500 = 4146$

Cost per unit clock cycle after improvement = Cost / Clock cycle time = $\frac{4146}{940} = 4.38$

Change in costs = $4.38 - 4.24 = 0.14$

Performance = $1/\text{Latency}$

Performance before improvements = $\frac{1}{100 * 930 * 10^{-12}} = 10.75 * 10^6$

Performance after improvements = $\frac{1}{97 * 940 * 10^{-12}} = 10.967 * 10^6$

Change in performance = $10.967 * 10^6 - 10.75 * 10^6 = 0.217 * 10^6$

Cost Ratio = $\frac{4.38}{4.24} = 1.03$

Performance Ratio = $\frac{10.967}{10.75} = 1.02$

We see that the performance ratio is **1.02** while the cost ratio is **1.03**

The Cost Ratio is higher than the Performance Ratio by **0.01**

(c) Given the cost/performance ratios you just calculated, describe a situation where it makes sense to add more registers and describe a situation where it doesn't make sense to add more registers.

If the priority is performance, adding more registers makes sense because adding more registers improve performance but increases cost. It streamlines instruction execution, enhancing overall system performance.

Contrastly, if cost reduction is the priority, adding more registers may not be wise. Using fewer registers lowers costs but can compromise performance, as it increases the number of instructions and affects latency negatively.

In summary, adding more registers is sensible when prioritizing performance, even with increased costs. However, if cost reduction is the main concern, adding more registers might not be the optimal choice due to potential performance trade-offs.

12.14.16

(a) What is the clock cycle time in a pipelined and nonpipelined processor?

For a pipelined processor

Instructions Decode = 350ps

Clock cycle time of pipelined processor = **350ps**

For a non-pipelined processor

Clock cycle = IF + ID + EX + MEM + WB = 250ps + 350ps + 150ps + 300ps + 200ps = **1250ps**

(b) What is the total latency of an lw instruction in a pipelined and non-pipelined processor?

For a pipelined processor

Total latency = # of cycles * clock cycles = 5 * 350ps = **1750ps**

For a non-pipelined processor

Total latency = IF + ID + EX + MEM + WB = 250ps + 350ps + 150ps + 300ps + 200ps = **1250ps**

(c) If we can split one stage of the pipelined datapath into two new stages, each with half the latency of the original stage, which stage would you split and what is the new clock cycle time of the processor?

I would split the longest stage as it would be the best way to reduce the cycle time. The new cycle time would then be calculated on the next longest stage. Currently the longest stage is ID, so the new longest cycle time would be MEM which is **300ps**

(d) Assuming there are no stalls or hazards, what is the utilization of the data memory?

Total utilization = Load instruction + store instruction

Total utilization = 20% + 15%

Total utilization = **35%**

(e) Assuming there are no stalls or hazards, what is the utilization of the write-register port of the "Registers" unit?

Utilization of the write-register port = LW utilization + ALU utilization = 20% + 45% = **65% Clock Cycles**